


# Physics 2250: Problem Set II

Jeremy Favro

September 20, 2024

**Problem 1.** ...

**Solution 1.**

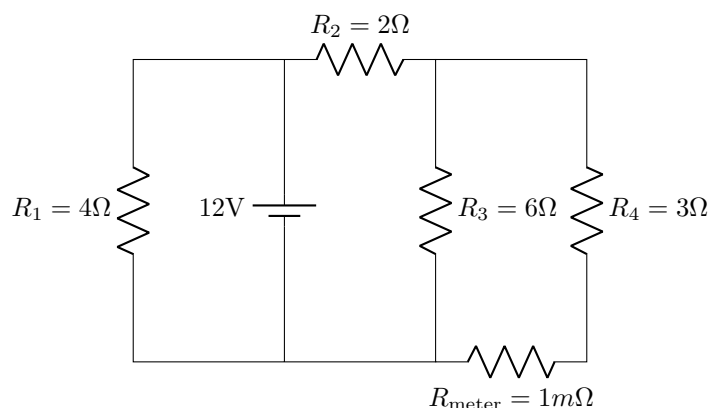


a) By simplifying to equivalent resistance and using Ohm's law in the loop containing  $\epsilon_a$  and  $\epsilon_b$  (without  $R_{\text{meter}}$ )  $I_{\text{tot}} = \frac{V}{R} = \frac{12\text{V}}{4\Omega} = 3\text{A}$  so by the current divider rule and KCL the current through  $R_4$  is the same as the current through points  $\epsilon_a$  and  $\epsilon_b$ ,  $I_{ab} = 3\text{A} \frac{6\Omega}{6\Omega + 3\Omega} = 2\text{A}$

b) This is effectively the same until the "second" (really the first one calculated) current divider  $\frac{6\Omega}{6\Omega + 3\Omega}$  because the branch we are calculating current for now contains the extra resistance of the meter and thus draws *very* slightly less current. The new current through this branch therefore becomes  $3\text{A} \frac{6\Omega}{6\Omega + 3.001\Omega} = 1.99978\text{A}$

**Problem 2.** The figure below displays a periodic current and potential delivered to some load (resistor). Note, the maximum values for  $v$  and  $i$  are 16V and 5A, respectively.

**Solution 2.**

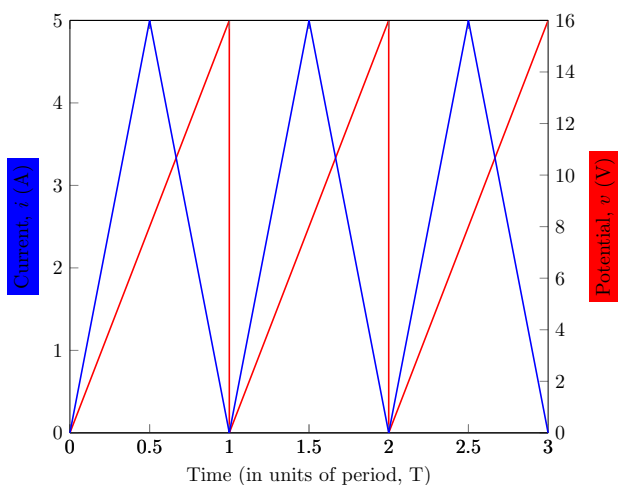

$$\text{a) } \bar{v}(t) = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \cdot \frac{1}{2} T \cdot 16V = 8V$$

$$\bar{i}(t) = \frac{1}{T} \int_0^T i(t) dt = \frac{1}{T} \cdot \frac{1}{2} T \cdot 5A = 2.5A$$

b) Voltage here can be expressed as a linear function  $v(t) = \frac{16}{T}t$  for one period so

$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{T} \cdot \frac{16^2}{T^2} \cdot \frac{T^3}{3}} = \frac{16\sqrt{3}}{3} \approx 9.238V$$

The same almost works for current  $i(t)$  but it has to be made piecewise to account for the downward slope from  $\frac{T}{2}$  to  $T$ , not that the sign really matters when doing the integration


$$i(t) = \begin{cases} \frac{5}{T}t & 0 \leq t \leq \frac{T}{2} \\ -\frac{5}{T}t & \frac{T}{2} \leq t \leq T \end{cases}$$

$$\text{which integrates as } i_{rms} = \sqrt{\frac{1}{T} \left[ \int_0^{\frac{T}{2}} i^2(t) dt + \int_{\frac{T}{2}}^T i^2(t) dt \right]} = \sqrt{\frac{1}{T} \cdot \frac{25}{T^2} \left[ \frac{T^3}{6} + \frac{T^3}{3} - \frac{T^3}{24} \right]} = \sqrt{\frac{25}{T} \cdot \frac{8T^2}{24}} = \frac{5\sqrt{3}}{3} \approx 2.887A$$

$$\text{c) } P_{avg} = v_{rms} i_{rms} = 26.67W$$

**Problem 3.** Consider the following network of capacitors

**Solution 3.**

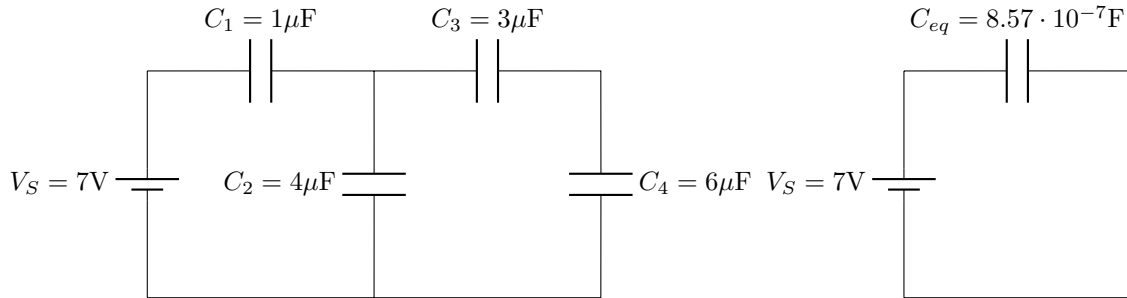

a) Capacitor  $C_{eq}$  must have a voltage drop of 7V to satisfy KVL therefore  $Q_{tot} = C_{eq}V = 6\mu C$ . Re-complicating the circuit and using  $Q_{tot}$  we can find that the voltage drop across  $C_1$  is  $V_{C1} = \frac{Q_{tot}}{C_1} = 6V$ . By KVL this means that the rest of the circuit must contribute a potential drop of 1V which means that  $C_2$  will experience a charge of  $Q_{C2} = 1V4\mu F = 4\mu C$  therefore because charge is conserved the  $C_3$ - $C_4$  branch experiences the rest of  $Q_{tot}$  or  $Q_{C3C4} = Q_{tot} - Q_{C2} = 2\mu C$ . Therefore the voltages across  $C_3$  &  $C_4$  are 0.6V & 0.3V respectively.

Capacitor	Charge	Voltage
$C_1$	$6\mu C$	6V
$C_2$	$4\mu C$	1V
$C_3$	$2\mu C$	0.6V
$C_4$	$2\mu C$	0.3V

b) Once at equilibrium we would see a voltage drop across  $C_1$  of 7V (so  $Q = C_1V = 7\mu C$ ) and no drop or charge across any other component because  $C_1$ , when fully charged, will act as a break in the circuit and not permit current to flow.