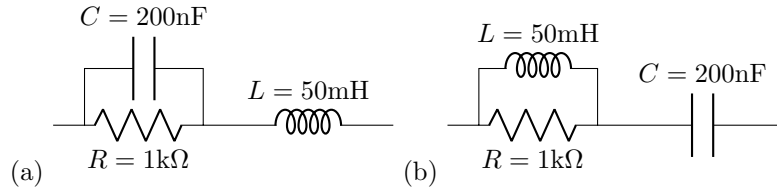


Physics 2250: Problem Set IX

Jeremy Favro

December 4, 2024

Problem 1. Determine both the DC impedance and the impedance at a frequency of $f = 1\text{kHz}$ of the circuits shown below.



Solution 1. Here $f = 1\text{kHz} \implies \omega = 2000\pi\text{rad s}^{-1}$

(a)

$$\begin{aligned}
 Z &= \left(\frac{1}{R} + j\omega C \right)^{-1} + j\omega L \\
 &= \frac{R}{1 + j\omega CR} + j\omega L \\
 &= \frac{R + (j\omega L)(1 + j\omega CR)}{1 + j\omega CR} \\
 &= \frac{R(1 - j\omega CR) + (j\omega L)(1 + (\omega CR)^2)}{1 + (\omega CR)^2} \\
 &= \frac{R - j\omega CR^2 + j\omega L + j\omega L(\omega CR)^2}{1 + (\omega CR)^2} \\
 &= \frac{R}{1 + (\omega CR)^2} + \frac{-\omega CR^2 + \omega L + \omega L(\omega CR)^2}{1 + (\omega CR)^2}j
 \end{aligned}$$

Which means that the DC impedance ($\omega = 0$) is just R , and impedance with a frequency of 1kHz is $\approx 91.9997 - 25.1338j\Omega$


(b)

$$\begin{aligned} Z &= \left(\frac{1}{R} + \frac{1}{j\omega L} \right)^{-1} + \frac{1}{j\omega C} \\ &= \frac{j\omega LR}{R + j\omega L} + \frac{1}{j\omega C} \\ &= \frac{j\omega LR^2 + (\omega L)^2 R}{R^2 + (\omega L)^2} - \frac{j}{\omega C} \\ &= \frac{j\omega LR^2 (\omega C) + (\omega L)^2 R (\omega C)}{(\omega C) (R^2 + (\omega L)^2)} - \frac{j (R^2 + (\omega L)^2)}{(\omega C) (R^2 + (\omega L)^2)} \\ &= \frac{j\omega LR^2 (\omega C) + (\omega L)^2 R (\omega C) - (R^2 + (\omega L)^2) j}{(\omega C) (R^2 + (\omega L)^2)} \\ &= \frac{(\omega L)^2 R}{R^2 + (\omega L)^2} + \frac{L (\omega R)^2 C - (R^2 + (\omega L)^2)}{(\omega C) (R^2 + (\omega L)^2)} j \end{aligned}$$

Which means that the DC impedance is infinite, and the impedance at a frequency of 1kHz is $89.8302 - 32.2716j\Omega$

Problem 2. A purely sinusoidal voltage of $V_s(t)$ of amplitude 10V and frequency $\omega = 300\text{rad s}^{-1}$ is applied in the circuit shown below.

- (a) Find the equivalent circuit impedance, \tilde{Z}_{tot}
- (b) Find the total circuit current, $\tilde{I}(t)$
- (c) Find the average power expended in the circuit, and compare this to the DC power expended in the circuit (i.e. the power expended when powered by a simple 10V battery)

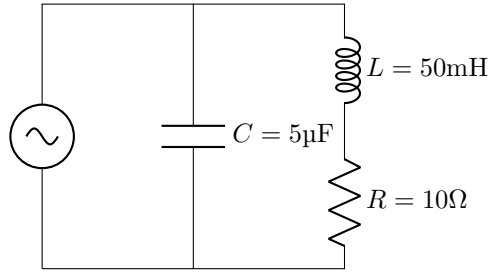

Solution 2.

(a)

$$\begin{aligned}
Z &= \left(j\omega C + \frac{1}{R + j\omega L} \right)^{-1} \\
&= \left(\frac{1 + (R + j\omega L) j\omega C}{R + j\omega L} \right)^{-1} \\
&= \frac{R + j\omega L}{1 + (R + j\omega L) j\omega C} \\
&= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega CR} \\
&= \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega CR)}{(1 - \omega^2 LC)^2 + (\omega CR)^2} \\
&= \frac{j\omega L - j\omega^3 L^2 C + \omega^2 LRC + R - \omega^2 LRC - j\omega CR^2}{(1 - \omega^2 LC)^2 + (\omega CR)^2} \\
&= \frac{j\omega L - j\omega^3 L^2 C - j\omega CR^2 + R}{(1 - \omega^2 LC)^2 + (\omega CR)^2} \\
&= \frac{R}{(1 - \omega^2 LC)^2 + (\omega CR)^2} + \frac{\omega L - \omega^3 L^2 C - \omega CR^2}{(1 - \omega^2 LC)^2 + (\omega CR)^2} j \\
&= 10.4632 + 15.5367i\Omega
\end{aligned}$$

In phasor notation this is $\sqrt{10.4632^2 + 15.5367^2} e^{i \arctan(\frac{15.5367}{10.4632})} = 18.7315 e^{0.9782j}$

(b) $V_s(t)$ in phasor notation is $10e^{300tj}$


$$\begin{aligned}
\tilde{I}(t) &= \frac{V_s(t)}{\tilde{Z}_{tot}} \\
\tilde{I}(t) &= \frac{10e^{300tj}}{18.7315e^{0.9782j}} \\
\tilde{I}(t) &= 0.5339e^{(300t-0.9782)j}
\end{aligned}$$

(c)

$$\begin{aligned}
\langle P \rangle &= \frac{1}{2} \text{Re} [V(t) \tilde{I}^*(t)] \\
&= \frac{1}{2} \text{Re} [10e^{300tj} \cdot 0.5339e^{-j(300t-0.9782)}] \\
&= \frac{1}{2} \text{Re} [5.339e^{0.9782j}] \\
&= 2.6695 \text{Re} [\cos(0.9782) + j \sin(0.9782)] \\
&= 1.4909\text{W}
\end{aligned}$$

DC power is just $P = \frac{V^2}{R} = \frac{10V^2}{10\Omega} = 10\text{W}$

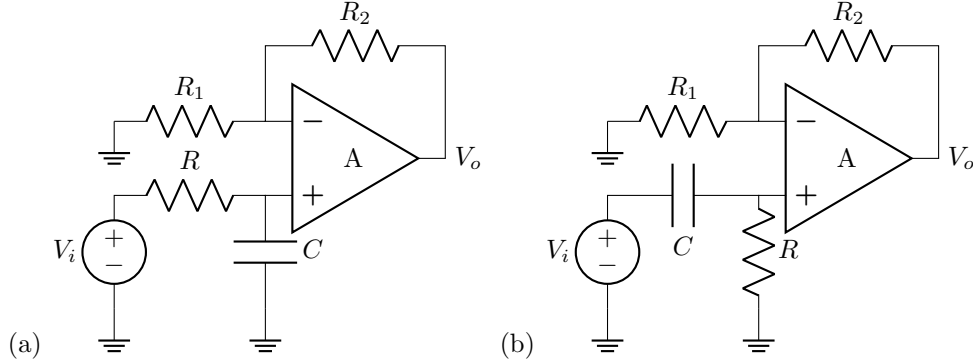Problem 3. Consider the two Op-Amp filter circuits shown below. Each has a sinusoidal input, V_i , and component values of $C = 500\text{nF}$, $R = 1\text{k}\Omega$, $R_1 = 100\Omega$, $R_2 = 10\text{k}\Omega$.



For each filter:

- Use qualitative reasoning to predict the output (V_o) at low and at high input frequencies to determine the broad filter type.
- Find analytical expressions for
 - The output voltage in terms of the input voltage, $V_o(V_i)$.
 - The magnitude of the output relative to the input, $\left|\frac{V_o}{V_i}\right|$.
 - The phase difference between the output and input, $\Delta\phi_{V_o-V_i}$.
- Use any software of your choice to plot $\left|\frac{V_o}{V_i}\right|$ and $\Delta\phi_{V_o-V_i}$ for frequencies up to $\omega = 2\text{MHz}$. Make sure to annotate your plots with proper and legible labels. Plot $\left|\frac{V_o}{V_i}\right|$ on a log-log scale and $\Delta\phi_{V_o-V_i}$ on a linear-log scale.
- Find the (exact or approximate) frequency and phase difference at which $\left|\frac{V_o}{V_i}\right| = 1$.

Solution 3.

- At $\omega = 0$ in filter (a) the capacitor acts like an open meaning that the op-amp is in a non-inverting configuration where $V_o = \left(1 + \frac{R_2}{R_1}\right) V_i = 101V_i$. As $\omega \rightarrow \infty$ in filter (a) the capacitor acts like a wire, meaning the op-amp does nothing so $V_o = 0$. So, filter (a) is a low pass filter with some gain. In filter (b) at $\omega = 0$ the capacitor acts like an open, dropping all of V_i , meaning that $V_o = 0$. As $\omega \rightarrow \infty$ the capacitor acts like a wire meaning that the op-amp is in a non-inverting configuration where $V_o = \left(1 + \frac{R_2}{R_1}\right) V_i = 101V_i$. So, filter (b) is a high pass filter with some gain.
- The output voltage in terms of the input voltage, $V_o(V_i)$.
 - The magnitude of the output relative to the input, $\left|\frac{V_o}{V_i}\right|$.
 - The phase difference between the output and input, $\Delta\phi_{V_o-V_i}$.
- Use any software of your choice to plot $\left|\frac{V_o}{V_i}\right|$ and $\Delta\phi_{V_o-V_i}$ for frequencies up to $\omega = 2\text{MHz}$. Make sure to annotate your plots with proper and legible labels. Plot $\left|\frac{V_o}{V_i}\right|$ on a log-log scale and $\Delta\phi_{V_o-V_i}$ on a linear-log scale.
- Find the (exact or approximate) frequency and phase difference at which $\left|\frac{V_o}{V_i}\right| = 1$.