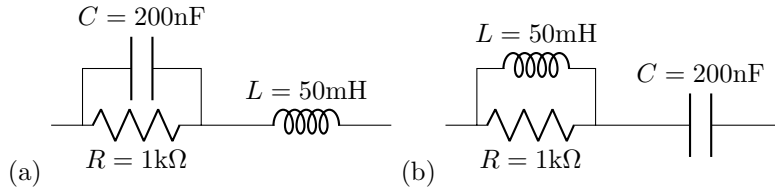


Physics 2250: Problem Set IX

Jeremy Favro

December 5, 2024

Problem 1. Determine both the DC impedance and the impedance at a frequency of $f = 1\text{kHz}$ of the circuits shown below.



Solution 1. Here $f = 1\text{kHz} \implies \omega = 2000\pi\text{rad s}^{-1}$

(a)

$$\begin{aligned}
 Z &= \left(\frac{1}{R} + j\omega C \right)^{-1} + j\omega L \\
 &= \frac{R}{1 + j\omega CR} + j\omega L \\
 &= \frac{R + (j\omega L)(1 + j\omega CR)}{1 + j\omega CR} \\
 &= \frac{R(1 - j\omega CR) + (j\omega L)(1 + (\omega CR)^2)}{1 + (\omega CR)^2} \\
 &= \frac{R - j\omega CR^2 + j\omega L + j\omega L(\omega CR)^2}{1 + (\omega CR)^2} \\
 &= \frac{R}{1 + (\omega CR)^2} + \frac{-\omega CR^2 + \omega L + \omega L(\omega CR)^2}{1 + (\omega CR)^2}j
 \end{aligned}$$

Which means that the DC impedance ($\omega = 0$) is just R , and impedance with a frequency of 1kHz is $\approx 91.9997 - 25.1338j\Omega$


(b)

$$\begin{aligned} Z &= \left(\frac{1}{R} + \frac{1}{j\omega L} \right)^{-1} + \frac{1}{j\omega C} \\ &= \frac{j\omega LR}{R + j\omega L} + \frac{1}{j\omega C} \\ &= \frac{j\omega LR^2 + (\omega L)^2 R}{R^2 + (\omega L)^2} - \frac{j}{\omega C} \\ &= \frac{j\omega LR^2 (\omega C) + (\omega L)^2 R (\omega C)}{(\omega C) (R^2 + (\omega L)^2)} - \frac{j (R^2 + (\omega L)^2)}{(\omega C) (R^2 + (\omega L)^2)} \\ &= \frac{j\omega LR^2 (\omega C) + (\omega L)^2 R (\omega C) - (R^2 + (\omega L)^2) j}{(\omega C) (R^2 + (\omega L)^2)} \\ &= \frac{(\omega L)^2 R}{R^2 + (\omega L)^2} + \frac{L (\omega R)^2 C - (R^2 + (\omega L)^2)}{(\omega C) (R^2 + (\omega L)^2)} j \end{aligned}$$

Which means that the DC impedance is infinite, and the impedance at a frequency of 1kHz is $89.8302 - 32.2716j\Omega$

Problem 2. A purely sinusoidal voltage of $V_s(t)$ of amplitude 10V and frequency $\omega = 300\text{rad s}^{-1}$ is applied in the circuit shown below.

- (a) Find the equivalent circuit impedance, \tilde{Z}_{tot}
- (b) Find the total circuit current, $\tilde{I}(t)$
- (c) Find the average power expended in the circuit, and compare this to the DC power expended in the circuit (i.e. the power expended when powered by a simple 10V battery)

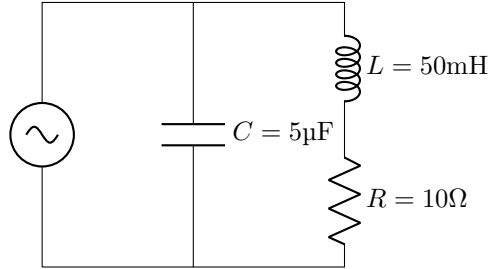

Solution 2.

(a)

$$\begin{aligned}
Z &= \left(j\omega C + \frac{1}{R + j\omega L} \right)^{-1} \\
&= \left(\frac{1 + (R + j\omega L) j\omega C}{R + j\omega L} \right)^{-1} \\
&= \frac{R + j\omega L}{1 + (R + j\omega L) j\omega C} \\
&= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega CR} \\
&= \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega CR)}{(1 - \omega^2 LC)^2 + (\omega CR)^2} \\
&= \frac{j\omega L - j\omega^3 L^2 C + \omega^2 LRC + R - \omega^2 LRC - j\omega CR^2}{(1 - \omega^2 LC)^2 + (\omega CR)^2} \\
&= \frac{j\omega L - j\omega^3 L^2 C - j\omega CR^2 + R}{(1 - \omega^2 LC)^2 + (\omega CR)^2} \\
&= \frac{R}{(1 - \omega^2 LC)^2 + (\omega CR)^2} + \frac{\omega L - \omega^3 L^2 C - \omega CR^2}{(1 - \omega^2 LC)^2 + (\omega CR)^2} j \\
&= 10.4632 + 15.5367i\Omega
\end{aligned}$$

In phasor notation this is $\sqrt{10.4632^2 + 15.5367^2} e^{i \arctan(\frac{15.5367}{10.4632})} = 18.7315 e^{0.9782j}$

(b) $V_s(t)$ in phasor notation is $10e^{300tj}$


$$\begin{aligned}
\tilde{I}(t) &= \frac{\tilde{V}_s(t)}{\tilde{Z}_{tot}} \\
\tilde{I}(t) &= \frac{10e^{300tj}}{18.7315e^{0.9782j}} \\
\tilde{I}(t) &= 0.5339e^{(300t-0.9782)j}
\end{aligned}$$

(c)

$$\begin{aligned}
\langle P \rangle &= \frac{1}{2} \text{Re} \left[\tilde{V}_s(t) \tilde{I}^*(t) \right] \\
&= \frac{1}{2} \text{Re} \left[10e^{300tj} \cdot 0.5339e^{-j(300t-0.9782)} \right] \\
&= \frac{1}{2} \text{Re} \left[5.339e^{0.9782j} \right] \\
&= 2.6695 \text{Re} [\cos(0.9782) + j \sin(0.9782)] \\
&= 1.4909\text{W}
\end{aligned}$$

DC power is just $P = \frac{V^2}{R} = \frac{10V^2}{10\Omega} = 10\text{W}$

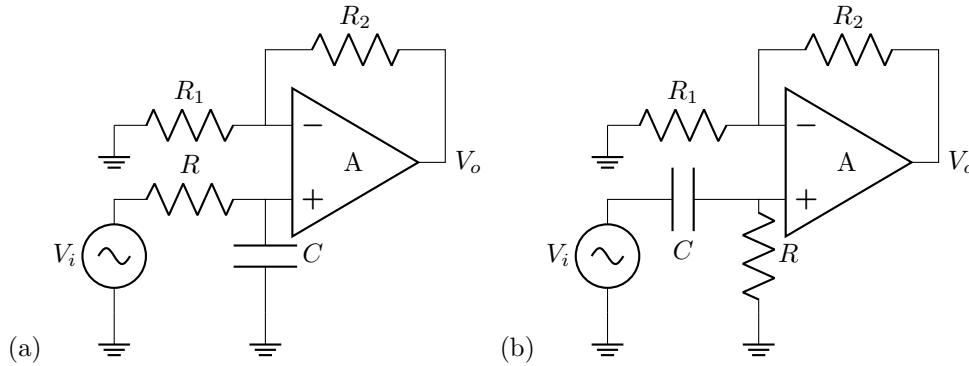Problem 3. Consider the two Op-Amp filter circuits shown below. Each has a sinusoidal input, V_i , and component values of $C = 500\text{nF}$, $R = 1\text{k}\Omega$, $R_1 = 100\Omega$, $R_2 = 10\text{k}\Omega$.




For each filter:

- Use qualitative reasoning to predict the output (V_o) at low and at high input frequencies to determine the broad filter type.
- Find analytical expressions for
 - The output voltage in terms of the input voltage, $V_o(V_i)$.
 - The magnitude of the output relative to the input, $\left|\frac{V_o}{V_i}\right|$.
 - The phase difference between the output and input, $\Delta\phi_{V_o-V_i}$.
- Use any software of your choice to plot $\left|\frac{V_o}{V_i}\right|$ and $\Delta\phi_{V_o-V_i}$ for frequencies up to $\omega = 2\text{MHz}$. Make sure to annotate your plots with proper and legible labels. Plot $\left|\frac{V_o}{V_i}\right|$ on a log-log scale and $\Delta\phi_{V_o-V_i}$ on a linear-log scale.
- Find the (exact or approximate) frequency and phase difference at which $\left|\frac{V_o}{V_i}\right| = 1$.

Solution 3.

- At $\omega = 0$ in filter (a) the capacitor acts like an open meaning that the op-amp is in a non-inverting configuration where $V_o = \left(1 + \frac{R_2}{R_1}\right) V_i = 101V_i$. As $\omega \rightarrow \infty$ in filter (a) the capacitor acts like a wire, meaning the op-amp does nothing so $V_o = 0$. So, filter (a) is a low pass filter with some gain. In filter (b) at $\omega = 0$ the capacitor acts like an open, dropping all of V_i , meaning that $V_o = 0$. As $\omega \rightarrow \infty$ the capacitor acts like a wire meaning that the op-amp is in a non-inverting configuration where $V_o = \left(1 + \frac{R_2}{R_1}\right) V_i = 101V_i$. So, filter (b) is a high pass filter with some gain.
- I'm separating this into one part per circuit so it doesn't get super cluttered.
 - Treating circuit (a) as a two stage circuit where the amplifier is a separate multiplier of 101 makes this conceptually much easier for me. To do this, I'll analyze the circuit below, finding $V'_o(V_i)$ and then just multiply V'_o by 101 to get V_o

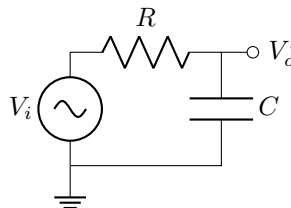

We're trying to find the voltage dropped across the capacitor here which is given by $V'_o = \tilde{I}(t)\tilde{Z}_C$. Here

$$\tilde{I}(t) = \frac{\tilde{V}_i(t)}{\tilde{Z}_R + \tilde{Z}_C} \text{ so}$$

$$\begin{aligned} V'_o &= \frac{\tilde{V}_i(t)\tilde{Z}_C}{\tilde{Z}_R + \tilde{Z}_C} \\ &= \frac{\tilde{V}_i(t) \left(-\frac{j}{\omega C}\right)}{R - \frac{j}{\omega C}} \\ &= \frac{\tilde{V}_i(t) [(\omega C)^{-2} - R(\omega C)^{-1}j]}{R^2 + (\omega C)^{-2}} \\ &= \frac{\tilde{V}_i(t)(\omega C)^{-2}}{R^2 + (\omega C)^{-2}} - \frac{\tilde{V}_i(t)R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \\ \therefore V_o &= 101\tilde{V}_i(t) \left[\frac{(\omega C)^{-2}}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right] \end{aligned}$$


ii(a).

$$\begin{aligned} &= 101 \left| \frac{\cancel{\tilde{V}_i(t)} \left[\frac{(\omega C)^{-2}}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right]}{\cancel{\tilde{V}_i(t)}} \right| \\ &= 101 \sqrt{\left(\frac{(\omega C)^{-2}}{R^2 + (\omega C)^{-2}} \right)^2 + \left(\frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}} \right)^2} \\ &= \frac{101}{R^2 + (\omega C)^{-2}} \sqrt{(\omega C)^{-4} + R^2(\omega C)^{-2}} \\ &= \frac{101}{(\omega C)(R^2 + (\omega C)^{-2})} \sqrt{\frac{1}{(\omega C)^2} + R^2} \\ &= \frac{101\sqrt{1 + R^2(\omega C)^2}}{(\omega C)^2 (R^2 + (\omega C)^{-2})} \end{aligned}$$

iii(a).

$$\begin{aligned} \Delta\phi_{V_o-V_i} &= \arctan \left(\frac{\text{Im} \left[\frac{\tilde{V}_o(t)}{\tilde{V}_i(t)} \right]}{\text{Re} \left[\frac{\tilde{V}_o(t)}{\tilde{V}_i(t)} \right]} \right) \\ &= \arctan \left(\frac{\text{Im} \left[\frac{(\omega C)^{-2}}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right]}{\text{Re} \left[\frac{(\omega C)^{-2}}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right]} \right) \\ &= \arctan \left(\frac{-\frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}}{\frac{(\omega C)^{-2}}{R^2 + (\omega C)^{-2}}} \right) \\ &= \arctan(-R\omega C) \end{aligned}$$

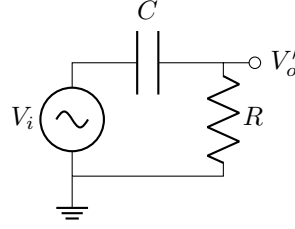- i(b). Treating circuit (b) as a two stage circuit where the amplifier is a separate multiplier of 101 makes this conceptually much easier for me. To do this, I'll analyze the circuit below, finding $V'_o(V_i)$ and then just multiply V'_o by 101 to get V_o



We're trying to find the voltage dropped across the capacitor here which is given by $V'_o = \tilde{I}(t)\tilde{Z}_R$. Here

$$\tilde{I}(t) = \frac{\tilde{V}_i(t)}{\tilde{Z}_R + \tilde{Z}_C} \text{ so}$$

$$V'_o = \frac{\tilde{V}_i(t)\tilde{Z}_R}{\tilde{Z}_R + \tilde{Z}_C}$$

$$V'_o = \frac{\tilde{V}_i(t)R}{R - j(\omega C)^{-1}}$$

$$V'_o = \tilde{V}_i(t) \frac{R^2 - jR(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}$$

$$V'_o = \tilde{V}_i(t) \left[\frac{R^2}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right]$$

$$\therefore V_o = 101\tilde{V}_i(t) \left[\frac{R^2}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right]$$

ii(b).


$$\begin{aligned} &= 101 \left| \frac{R^2}{R^2 + (\omega C)^{-2}} - \frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}j \right| \\ &= \frac{101}{R^2 + (\omega C)^{-2}} \sqrt{(R^2)^2 + (R(\omega C)^{-1})^2} \\ &= \frac{101}{R^2 + (\omega C)^{-2}} \sqrt{\frac{R^4(\omega C)^{-2} + R^2(\omega C)^{-2}}{(\omega C)^{-2}}} \\ &= \frac{101R\sqrt{1 + R^2}}{R^2 + (\omega C)^{-2}} \end{aligned}$$

iii(b).


$$\begin{aligned} \Delta\phi_{V_o - V_i} &= \arctan \left(\frac{\text{Im} \left[\frac{\tilde{V}_o(t)}{\tilde{V}_i(t)} \right]}{\text{Re} \left[\frac{\tilde{V}_o(t)}{\tilde{V}_i(t)} \right]} \right) \\ &= \arctan \left(\frac{-\frac{R(\omega C)^{-1}}{R^2 + (\omega C)^{-2}}}{\frac{R^2}{R^2 + (\omega C)^{-2}}} \right) \\ &= \arctan \left(-\frac{1}{R\omega C} \right) \end{aligned}$$

(c) Plotted with TikZ


$\left| \frac{V_o}{V_i} \right|$ as a function of frequency for an active low-pass filter
(circuit (a))

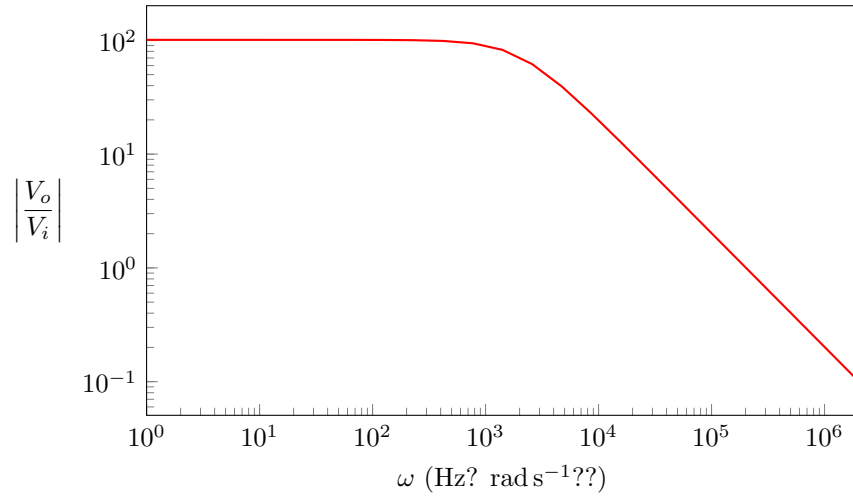

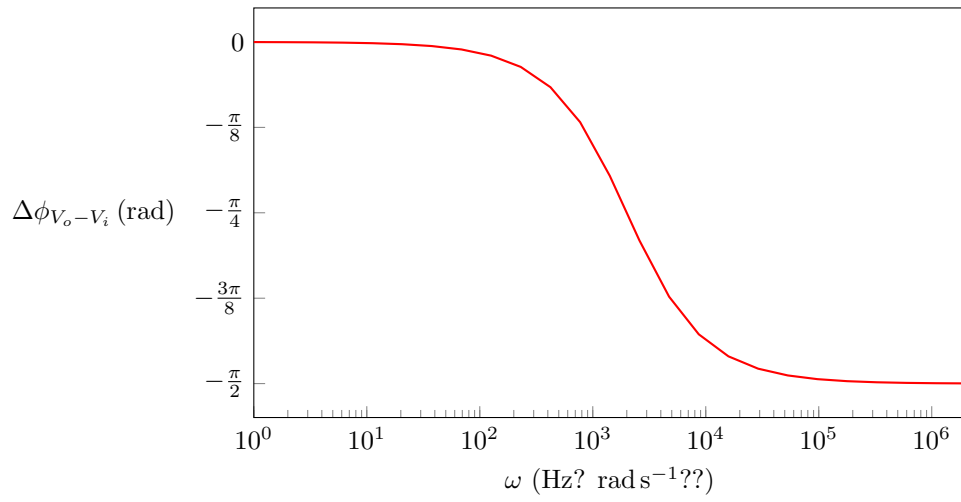
$\Delta\phi_{V_o-V_i}$ as a function of frequency for an active low-pass filter
(circuit (a))



$\left| \frac{V_o}{V_i} \right|$ as a function of frequency for an active high-pass filter
(circuit (b))

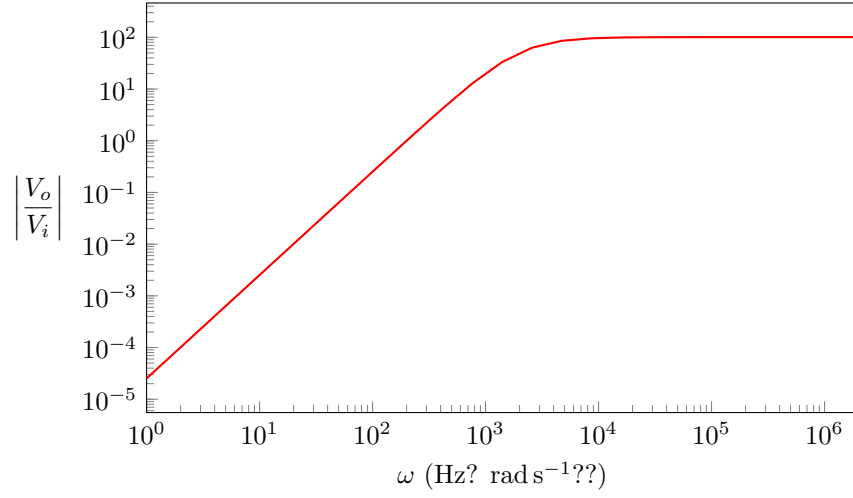

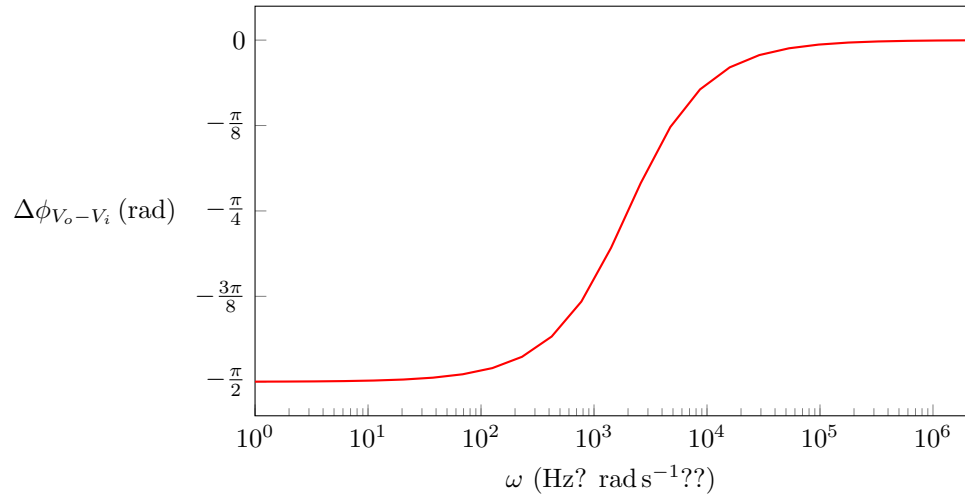$\Delta\phi_{V_o-V_i}$ as a function of frequency for an active high-pass filter
(circuit (b))



(d) For circuit (a)

$$1 = \frac{101\sqrt{1 + R^2(\omega C)^2}}{(\omega C)^2(R^2 + (\omega C)^{-2})}$$

$$(\omega C)^2 R^2 + 1 = 101\sqrt{1 + R^2(\omega C)^2}$$

$$\frac{(\omega C)^2 R^2 + 1}{\sqrt{1 + R^2(\omega C)^2}} = 101$$

$$\omega = \sqrt{\frac{101^2 - 1}{(RC)^2}} = 201990 \text{ whatever the unit of the graph above is}$$

For circuit (b)

$$1 = \frac{101R\sqrt{1+R^2}}{R^2 + (\omega C)^{-2}}$$

$$R^2 + (\omega C)^{-2} = 101R\sqrt{1+R^2}$$

$$\omega = \sqrt{\frac{1}{101RC^2\sqrt{1+R^2} - (RC)^2}} \approx 200$$