

Electronics Cheat Sheet

Jeremy Favro
October 30, 2024
Revision 1

Miscellaneous

Time Constants

For capacitors $V_C = V_s \left[1 - e^{-\frac{t}{RC}} \right]$

$$V_R = V_s e^{-\frac{t}{RC}}$$

And for inductors $V_R = V_s \left[1 - e^{-\frac{tR}{L}} \right]$

$$V_L = V_s e^{-\frac{tR}{L}}$$

Thévenin

Solve circuit for voltage across port ($V_A - V_B$), solve for equivalent resistance by replacing batteries with wires and current sources with opens and trace a current path from A to B. Put the voltage source in **series** with the equivalent resistor.

Norton

Short the port and find the current through the port short. Find resistance using the same method as Thévenin. Put the current source in **parallel** (across the port) with the equivalent resistor.


Differentials

$$V_R = IR = R \frac{dQ}{dt}$$

$$V_L = L \frac{dI}{dt} = L \frac{d^2Q}{dt^2}$$


$$V_C = \frac{Q}{C}$$

Diode

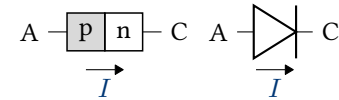


Op-Amps


Inverting Amplifier

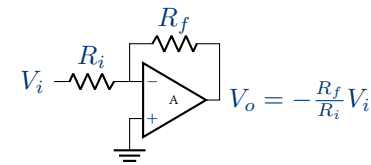


Non-Inverting Amplifier

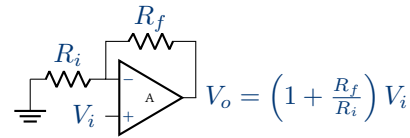


Voltage Follower

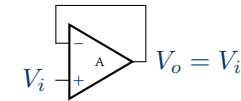


(Inverting) Adder

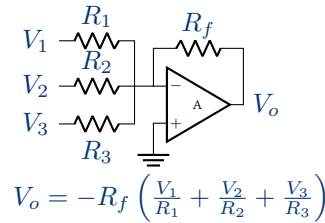

Subtractor

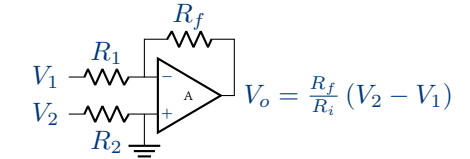

Integrator

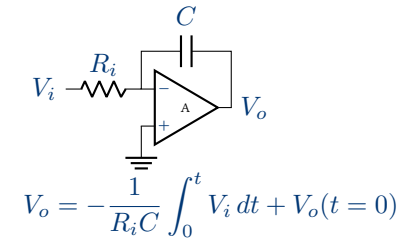

Differentiator

