

# Physics 2250: Problem Set I

Jeremy Favro


September 13, 2024

**Problem 1.** Determine the resistance of resistors A and B in the figure (not included here) below. (A: Red, Red, Red, Red; B: Blue, Violet, Green, Brown).

**Solution 1.** A:  $2.2 \cdot 100\Omega \pm 2\% = 2.2\text{k}\Omega \pm 44\Omega$ ; B:  $6.7 \cdot 100000\Omega \pm 1\% = 6.7\text{M}\Omega \pm 6.7\text{k}\Omega$

**Problem 2.** Consider the 5-resistor circuit shown below. Redrawn using circuitikz for ease of labeling in L<sup>A</sup>T<sub>E</sub>X

**Solution 2.**

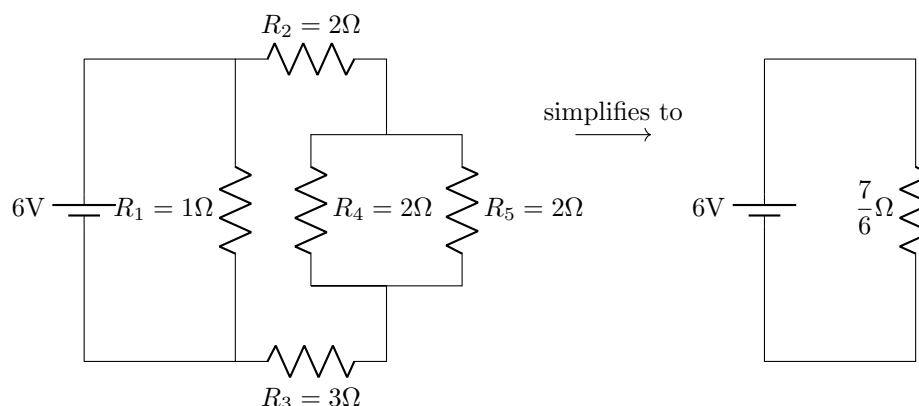


So,  $V = 6\text{V}$ ;  $R_{tot} = \frac{7}{6}\Omega \therefore I_{tot} = 7\text{A}$ .

a)  $P = IV = 7\text{A} \cdot 6\text{V} = 42\text{W}$

b) By the current divider rule the current entering  $R_1$  is  $I_{tot} \cdot \frac{R_2 + (\frac{1}{R_4} + \frac{1}{R_5})^{-1} + R_3}{R_{tot}} = 7\text{A} \cdot \frac{6\Omega}{7\Omega} = 6\text{A}$  which means that 1A enters  $R_2$  and is evenly split between  $R_4$  and  $R_5$  which both cause a voltage drop of  $0.5\text{A} \cdot 2\Omega = 1\text{V}$  because they are of equivalent resistance and by Kirchoff's junction law  $R_3$  therefore experiences the same 1A of current as  $R_2$ .

**Problem 3.** Consider the network shown below. Again redrawn in circuitikz (the voltage drop arrow almost clipping is killing me).

**Solution 3.**

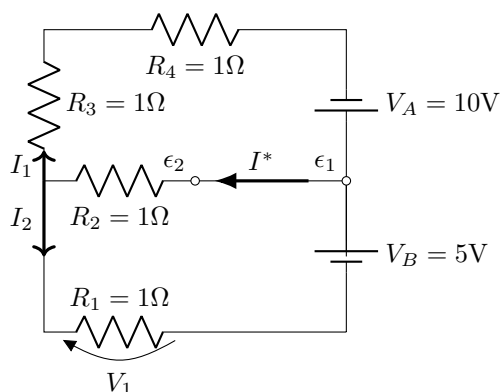

a) Going around the upper loop clockwise and the lower loop counter-clockwise starting at  $\epsilon_1$  we get  $-I^*R_2 - I_1R_3 - I_1R_4 + V_A = 0$  for the upper loop and  $-I^* - I_2R_1 + V_B = 0$  for the lower loop. By KCL we know that  $I^* = I_1 + I_2$ . Solving the upper loop equation for  $I_1$  we get that  $I_1 = \frac{-I^* + 10V}{2\Omega}$ . Doing the same for the lower loop equation we get that  $I_2 = -I^* + 5$ . Therefore

$$\begin{aligned} I^* &= \frac{-I^* + 10V}{2\Omega} - I^* + 5V \\ 2\Omega I^* &= -I^* + 10V - 2\Omega I^* + 10V \\ 2\Omega I^* &= -3\Omega I^* + 20V \\ 5\Omega I^* &= 20V \\ I^* &= 4A \end{aligned}$$


So  $I^*$  is 4 Amps in the direction of the loops at  $\epsilon_1$  (towards  $R_2$ )

b) 0V, I think? There's no resistor or anything there, and a wire is to be treated as having zero resistance so it would have zero voltage drop by Ohm's law.

c) Now that we know  $I^*$  we can solve the loop equations to get that  $I_1 = 3A$  &  $I_2 = 1A$  so the voltage drop across  $R_1$  is  $V = I_2R_1 = 1V$

**Problem 4. [BONUS]** If the source voltage in the figure below is  $V_S = 12V$ , what is the potential at node  $\epsilon$ ?

**Solution 4.**

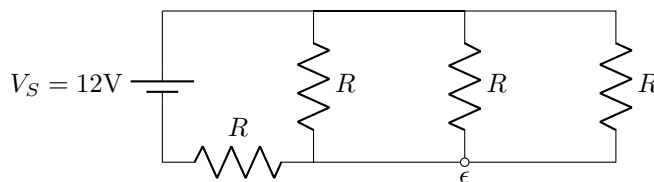

$$\epsilon = V_S - I_{tot} R_{before \epsilon}$$

$$R_{eq} = \left( \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right)^{-1} + R$$

$$R_{eq} = \frac{4R}{3} \Omega$$

$$I_{tot} = \frac{V_S}{R_{eq}}$$

$$I_{tot} = \frac{12V}{\frac{4R}{3} \Omega}$$

$$I_{tot} = \frac{9}{R} A$$

$$\epsilon = 12V - \frac{9}{R} A \frac{R}{3} \Omega$$

$$\epsilon = 9V$$